

CONTENTS

List of Tables	xvii	<i>Do-it-yourself testing; Overload to failure</i>
Preface	xix	1x.2.7 Resistor dividers 26 1x.2.8 “Digital” Resistors 28
ONE: Real-World Passive Components	1	<i>The digipot zoo; Digipot cautions; Wrapup</i>
1x.1 Wire and Connectors	5	1x.3 Capacitors 34 1x.3.1 Temperature coefficient 34 1x.3.2 ESR 35 1x.3.3 ESL 36 1x.3.4 Dissipation factor 37 1x.3.5 Voltage coefficient of capacitance 38 1x.3.6 AC voltage coefficient 40 1x.3.7 Aging 40 1x.3.8 Frequency dependence of capacitance 40 1x.3.9 Electromechanical self-resonance and microphonics 40 1x.3.10 Dielectric absorption 42 1x.3.11 Capacitor choices for typical applications 42 <i>Bypass and decoupling; Oscillators, filters, and timing; High frequency; Energy storage; AC line filtering; High voltage</i>
1x.1.1 Wire gauge: resistance, heating, and current-carrying capacity	5	1x.3.12 Capacitor miscellany 44
1x.1.2 Stranding, insulation, and tinning	5	1x.4 Inductors 46 1x.4.1 The basics 46 1x.4.2 Air-core inductors 46 <i>Solenoid – approximate; Solenoid – exact; Toroid; Loop</i>
1x.1.3 Printed circuit wiring	6	1x.4.3 Magnetic-core inductors 49 <i>Ferromagnetic materials; Ferrite-core solenoid; Ferrite-core toroid; Gapped core; Noise and spike suppression</i>
1x.1.4 PCB traces	7	
<i>Resistance and current-carrying capacity; Capacitance and inductance; Transmission-line impedance and attenuation</i>		
Transmission-line impedance and attenuation	7	
1x.1.5 Cable configurations	9	
1x.1.6 Inductance and skin effect	10	
<i>Inductance; Skin effect</i>		
1x.1.7 Capacitive and magnetic coupling	12	
1x.1.8 Mitigation of coupled signals	13	
1x.1.9 Shielded enclosures	13	
1x.1.10 Connectors	15	
1x.1.11 Connectors for RF and high-speed signals	17	
1x.1.12 High-density connectors	18	
1x.1.13 Connector miscellany	19	
1x.2 Resistors	20	
1x.2.1 Temperature coefficient	20	
1x.2.2 Self-capacitance and self-inductance	20	
1x.2.3 Nonlinearity (voltage coefficient)	21	
1x.2.4 Excess noise	22	
1x.2.5 Current-sense resistors and Kelvin connection	23	
1x.2.6 Power-handling capability and transient power	23	

1x.4.4	Inductors and transformers for power converters	58	TWO: Advanced BJT Topics	96
1x.4.5	Why build it, when you can buy it?	58	2x.1 What's the <i>Actual</i> Leakage Current of BJTs and JFETs?	102
1x.4.6	Inductor examples <i>Radiofrequency “chokes” and bias-T’s</i>	59	2x.2 Current-Source Problems and Fixes	103
1x.5	Poles and Zeros, and the “ <i>s</i> -Plane”	65	2x.2.1 Improving current-source performance	103
1x.6	Mechanical Switches and Relays	68	2x.2.2 Current mirrors: multiple outputs and current ratios	105
1x.6.1	Why use <i>mechanical</i> switches or relays?	68	2x.2.3 Widlar logarithmic current mirror	105
1x.6.2	So what's the problem? <i>Relay and switch contact life; Contact protection; Relay coil suppression; Improving relay switching speed</i>	68	2x.2.4 Current source from Widlar mirror	106
1x.6.3	Other switch and relay parameters <i>Switches: Function, actuator, bushing, terminals; Relays: Moving-armature, reed, and solid-state</i>	75	2x.3 The Cascode Configuration	108
1x.7	Diodes	77	2x.4 BJT Amplifier Distortion: a SPICE Exploration	110
1x.7.1	Diode characteristics <i>The family tree; Reverse (leakage) current; Forward voltage drop; Dynamic impedance; Peak current; Reverse capacitance; Zener capacitance</i>	77	2x.4.1 Grounded-emitter amplifier	110
1x.7.2	Stored charge and reverse recovery <i>Reverse recovery test circuit; Dependence on reverse and forward currents; Dependence on diode size; Schottky and fast-recovery diodes; Soft-recovery diodes; Step-recovery diodes; A far-out step-recovery application: Larkin's 40-amp kilovolt pulser; What about forward recovery?</i>	83	2x.4.2 Getting the model right	111
1x.7.3	The tunnel diode <i>Current versus voltage: Region of negative resistance; Measuring the tunnel diode characteristic curve; Tunnel diode trigger circuit</i>	89	2x.4.3 Exploring the linearity <i>Input–output transfer function; Gain versus input</i>	112
1x.8	Miscellaneous Circuits with Capacitors and Inductors	94	2x.4.4 Degenerated common-emitter amplifier	114
1x.8.1	Improved leading-edge detector	94	2x.4.5 Differential amplifier	114
1x.8.2	Capacitance multipliers	94	2x.4.6 Differential amplifier with emitter degeneration	116
			2x.4.7 Sziklai-connected differential amplifier	116
			2x.4.8 Sziklai-connected differential amplifier with current source	117
			2x.4.9 Sziklai-connected differential amplifier with cascode	118
			2x.4.10 Caprio's quad differential amplifier, with cascode	119
			2x.4.11 Caprio's quad with folded cascode – I	119
			2x.4.12 Caprio's quad with folded cascode – II	120
			2x.4.13 Measured distortion	121
			2x.4.14 Wrapup: amplifier modeling with SPICE	121
			2x.5 Early Effect and Early Voltage	122
			2x.5.1 Measuring Early effect	122
			2x.5.2 Some Early effect formulas	123
			2x.5.3 Consequences of Early effect: Output resistance	124
			<i>Maximum single-stage voltage gain; Current-source output impedance</i>	

2x.6	The Sziklai Configuration	126	2x.14.4	Epilogue: 120 V, 5 A, dc-10 MHz Laboratory Amplifier	152
2x.6.1	Two-transistor “standard” Sziklai	126		<i>Circuit details; Output protec-</i> <i>tion; Transistor choices</i>	
2x.6.2	Three-transistor “enhanced” Sziklai	126			
2x.6.3	Push-pull output stage: a Sziklai application	128	THREE: Advanced FET Topics	156	
2x.7	Bipolarity Current Mirrors	129	3x.1	A Guided Tour of JFETs	161
2x.7.1	A simple high-speed bipolarity current source <i>Reducing input current; Oper-</i> <i>ating at higher voltages</i>	129	3x.1.1	Gate current, I_{GSS} and I_G	166
2x.7.2	Precision bipolarity current source with folded cascode	131	3x.2	A Closer Look at JFET Transconduc-	
2x.8	The Emitter-Input Differential Amplifier	133	3x.2.1	Dependence of g_m on I_D	169
2x.8.1	An application: High-current, high-ratio current mirror	133	3x.2.2	Dependence of g_m on V_{DS}	170
2x.8.2	Improving the emitter-input differential amplifier	134	3x.2.3	Performance of the transconductance enhancer	171
2x.9	Transistor Beta versus Collector Current	136	3x.2.4	Transconductance in the JFET source follower	172
2x.10	Parasitic Oscillations in the Emitter Fol-	138	3x.3	Measuring JFET Transconductance	174
2x.11	lower	140	3x.4	A Closer Look at JFET Output Imp-	
2x.11.1	BJT Bandwidth and f_T Transistor amplifiers at high frequencies: first look <i>Reducing the effect of load ca-</i> <i>pacitance</i>	140	3x.4.1	edance	175
2x.11.2	High-frequency amplifiers: the ac model <i>ac model; Effects of collector voltage and current on transis-</i> <i>tor capacitances; Low- and high-</i> <i>current regions; SPICE par-</i> <i>ameters; Comparing SPICE mod-</i> <i>els with measured f_T; Wideband mi-</i> <i>cropower BJTs; Collector-base time constant and maximum os-</i> <i>cillation frequency</i>	140	3x.4.2	A JFET’s g_{os} -limited gain, G_{max}	175
2x.11.3	A high-frequency calculation example	145	3x.4.3	Source degeneration: another way to mitigate the g_{os} effect	176
2x.12	Two-terminal Negative Resistance Cir-	146	3x.4.4	Dependence of g_{os} on drain current density	177
2x.13	cuit	146	3x.4.5	Dependence of g_{os} and G_{max} on V_{DS}	178
2x.14	If It Quacks Like an Inducktor...	148	3x.4.6	A parting shot: g_{os} – sometimes it matters, sometimes it doesn’t	178
2x.14.1	“Designs by the Masters”: ± 20 V, 5 ns, 50 Ω Amplifier	150	3x.5	Example: A low-noise open-loop differential amplifier	178
2x.14.2	Output stage block diagram	150	MOSFETs as Linear Transistors	180	
2x.14.3	Output stage: the full enchilada	150	3x.5.1	Output characteristics and transfer function	180
		152		<i>Datasheet curves; Measured data</i>	
			3x.5.2	Linear operation: hotspot SOA limitation	182
			3x.5.3	Exploring the subthreshold region	182
				<i>MOSFETs at low drain voltage; MOSFETs at high drain voltage</i>	
			3x.5.4	Exploring a high-voltage MOSFET	185
				<i>IXTP1N120 transfer character-</i> <i>istics; IXTP1N120 transconduc-</i> <i>tance</i>	
			3x.5.5	SPICE models for power MOSFETs in the subthreshold region	187

3x.5.6	Typical SPICE model for a power MOSFET <i>Equivalent circuit; Model capacitances; Other models</i>	189	3x.11.2	The next 15 years <i>Logic-level gates; Packages; P-channel MOSFETs; High-voltage parts; Capacitances</i>	222
3x.5.7	An unusual low-voltage MOSFET	191	3x.11.3	Four kinds of power MOSFETs <i>Comparison of capacitances; Energy: what does all this capacitance stuff mean? Conclusion</i>	228
3x.6	Floating High-Voltage Current Sources	193	3x.12	Measuring MOSFET Gate Charge	233
3x.6.1	Raising output impedance with a cascode	193	3x.12.1	The gate charge curve depends on load current	233
3x.6.2	Reducing power dissipation	195	3x.12.2	Gate charge curves at constant load current	233
3x.6.3	Small-signal output impedance	195	3x.12.3	The gate charge curve depends also on drain voltage	234
3x.6.4	Low-cost predictable current source	196	3x.12.4	Gate charge test circuit	234
3x.6.5	Current sources for higher voltages <i>A simple scheme; Distributed series string; Some applications: HV amplifier; HV probe; High-voltage current sources: 250 µA; High-voltage current sources: 2 mA; Current sources in high-voltage amplifiers; High-voltage current sources: 5 mA and more; Perfect high-voltage current source</i>	197	3x.12.5	The Miller plateau	235
3x.7	Bandwidth of the Cascode; BJT versus FET	206	3x.13	Pulse Energy in Power MOSFETs	238
3x.7.1	The common-gate/common-base amplifier	206	3x.13.1	Limited only by maximum junction temperature <i>Controlled Conduction; Avalanche Mode</i>	238
3x.7.2	Cascode as common-gate/common-base amplifier	206	3x.13.2	Alternative graphs	240
3x.7.3	Estimating cascode bandwidth	207	3x.14	MOSFET Gate Drivers	242
3x.7.4	What about MOSFETs?	208	3x.15	High-Voltage Pulser	244
3x.7.5	Bandwidth of the source follower	208	3x.15.1	Two-switch +600 V pulser	244
3x.8	Bandwidth of the Source Follower with a Capacitive Load	209	3x.15.2	Two-switch +500 V 20 A fast pulser	246
3x.8.1	Follower with resistive signal source	209	3x.15.3	Two-switch reversible kilovolt pulser	247
3x.8.2	Follower driven with a current signal	210	3x.15.4	Output monitor	247
3x.9	High-Voltage Probe with High Input Impedance	213	3x.15.5	Three-switch bipolarity kilovolt pulser	249
3x.9.1	Compensated-offset MOSFET follower	213	3x.16	MOSFET ON-Resistance versus Temperature	251
3x.9.2	Bootstrapped op-amp follower	213	3x.17	Thyristors, IGBTs, and Wide-bandgap MOSFETs	252
3x.10	CMOS Linear Amplifiers	217	3x.17.1	Insulated-gate bipolar transistor (IGBT)	252
3x.11	MOSFETs Through the Ages	219	3x.17.2	Thyristors	252
3x.11.1	A MOSFET Saga: the First 30 Years	219	3x.17.3	Silicon carbide and gallium nitride MOSFETs	253
			3x.18	Power Transistors for Linear Amplifiers	254
			3x.19	Generating Fast High-Current LED Pulses	258
			3x.19.1	10 ns pulser	258
			3x.19.2	High-power pulser <i>Wiring; Gate voltage; Power dissipation</i>	258
			3x.19.3	Integrated LED Drivers	261

3x.20 Precision 1.5 kV 1 μ s Ramp	262	4x.4.1 Stability of the composite amplifier	299
3x.21 Fast Shutoff of High-Energy Magnetic Field	264	4x.4.2 Some more applications	300
3x.21.1 Helmholtz coils, rapid field shutoff	264	4x.4.3 Some cautions	302
3x.21.2 High voltage, high current switches	264	4x.5 High-Speed Op-amps I: Voltage Feedback	304
3x.22 Precision Charge-dispensing Piezo Positioner	266	4x.5.1 Voltage feedback and current feedback	304
3x.22.1 Fast MOSFET pulsed charge dispenser	266	<i>Some confusing terms</i>	
3x.22.2 Analog charge dispenser	268	4x.5.2 Overview of the table	305
3x.22.3 Small-step pulsed charge dispenser	269	4x.5.3 Scatterplots: Seeking trends	308
FOUR: Advanced Topics in Operational Amplifiers	271	4x.6 High-speed Op-amps II: Current Feedback	316
4x.1 From Philbrick to SMT	276	4x.6.1 Properties of CFBs	316
4x.2 Feedback Stability and Phase Margins	278	<i>Closed-loop bandwidth; Slew rate and output current; The feedback network and stability; Input current and precision</i>	
4x.2.1 Sliding f_2 : phase margin and circuit performance	279	4x.6.2 Care and feeding of CFBs	318
4x.2.2 What about amplifiers with $G_{CL} > 1$?	280	4x.6.3 “Hybrid” VFB+CFB op-amps	319
4x.2.3 Applying Bode plots to amplifier design	280	4x.6.4 When to use CFBs	320
4x.2.4 Afterword: High-speed op-amps <i>SPICEing the 3-pole op-amp</i>	281	4x.6.5 Mathematical postscript: bandwidth and gain in CFBs	320
4x.3 Transresistance Amplifiers	283	4x.6.6 Remarks on the table	321
4x.3.1 Stability problem	283	4x.7 Power Supply Rejection Ratio	324
4x.3.2 Stability solution	283	4x.8 Capacitive-Feedback Transimpedance Amplifiers	326
4x.3.3 An example: PIN diode amplifier <i>Gaining speed; “Pedal to the metal”; Sub-picofarad capacitors</i>	285	4x.8.1 Capacitive-feedback TIA for gigabit optical receivers	326
4x.3.4 A complete photodiode amplifier design	288	4x.9 Slew Rate: A Detailed Look	328
4x.3.5 Gain-switching	289	4x.9.1 Increasing slew rate	328
4x.3.6 Some loose ends	290	4x.9.2 Case study: high-voltage pulse generator	330
4x.3.7 Designs by the masters: A wide-range linear transimpedance amplifier	291	4x.10 Bias-Current Cancellation	332
4x.3.8 A “starlight-to-sunlight” linear photometer	293	4x.10.1 The best of both worlds?	332
4x.3.9 Autoranging wideband transimpedance amplifier	296	4x.10.2 Bias cancellation: the circuits	332
4x.3.10 Multiple-range cascode-bootstrap wideband TIA	297	<i>Simplest: Mirroring the base current of a cascode twin; Better: Bootstrapping the cascode bias; Another way: replicating the emitter current</i>	
4x.4 Unity-Gain Buffers	299	4x.10.3 Bias cancellation: how well does it work?	334
		4x.11 Rail-to-Rail Op-amps	336
		4x.11.1 Rail-to-rail inputs	336
		4x.11.2 Rail-to-rail outputs	336
		4x.11.3 Output near ground: when “RRO” isn’t	336
		4x.11.4 Offsetting the negative supply terminal	338

4x.11.5 Designs by the masters: the Monticelli output stage	339	4x.23.9 Faster HV amplifier: 1MHz and 1200V <i>Transistor choices; Circuit changes</i>	376
4x.12 Slewing and Settling	342	4x.24 High-Voltage Bipolarity Current Source	380
4x.12.1 Dependence on f_T <i>Slew-rate enhanced op-amps</i>	342	4x.24.1 Performance issues	381
4x.12.2 A caution: 'scope overdrive artifacts	343	4x.25 Ripple Reduction in PWM	383
4x.13 Resistorless Op-amp Gain Stage	346	4x.26 Nodal Loop Analysis: MOSFET Current Source	386
4x.14 Silicon Photomultipliers	348	4x.26.1 Example: MOSFET current source <i>Nodal model; KCL equations; Node equations; Results</i>	386
4x.14.1 SiPM characteristics	348	4x.26.2 Example: fast 2.5 A pulsed current	389
4x.14.2 SiPM construction	348		
4x.14.3 SiPM characteristics, electronics, and waveforms	349		
4x.15 External Current Limiting	351		
4x.16 Designs by the Masters: Bulletproof Input Protection	353		
4x.17 Canceling Base-Current Error in the Current Source	356	NINE: Advanced Topics in Power Control	391
4x.18 Analog "Function" Circuits	357	9x.1 Reverse Polarity Protection	396
4x.18.1 The Lorenz attractor	357	9x.2 Lithium-Ion Single-Cell Power Subsystem	397
4x.18.2 Summing amplifiers <i>Non-inverting Adder; Adder-subtractor</i>	357	9x.2.1 Charger features	397
4x.19 Normalizing Transimpedance Amplifier	360	9x.2.2 Monitor and Protect	397
4x.20 Logarithmic Amplifier	362	9x.2.3 Output voltage regulator	398
4x.20.1 Temperature compensation of gain	362	9x.2.4 Multiple cells: a "battery"	399
4x.21 A Circuit Cure for Diode Leakage	364	9x.3 Low-Voltage Boost Converters	400
4x.22 Capacitive Loads: Another View	365	9x.4 Foldback Current Limiting	402
4x.22.1 Frequency of oscillation	365	9x.5 PWM for DC Motors	403
4x.22.2 So, how about a few equations?	366	9x.5.1 The myth: PWM as secret sauce <i>An experiment; Toy trains and sewing machines; Another experiment</i>	403
4x.23 Precision High-Voltage Amplifier	368	9x.5.2 Wrapup: PWM versus dc for motor drive	405
4x.23.1 Overview	368	9x.5.3 Afterword: DC motor model <i>Series resistance: Op-amp analogy</i>	407
4x.23.2 High-voltage output stage	368	9x.6 Transformer + Rectifier + Capacitor = Giant Spikes!	410
4x.23.3 Front-end amplifier stage	370	9x.6.1 The effect	410
4x.23.4 Feedback stability	371	9x.6.2 Calculations and cures	410
4x.23.5 Circuit capacitances and capacitive loads <i>No load, no feedback capacitance; Add feedback capacitance; Add load capacitance; Output series resistor; SPICE analysis</i>	372	9x.7 Low-Voltage Clamp/Crowbar	412
4x.23.6 Output slew rate	374	9x.7.1 New clamp/crowbar <i>Circuit operation; Additional details; Performance</i>	412
4x.23.7 Measured performance	374	9x.8 High-Efficiency ("Green") Switching Power Supplies	415
4x.23.8 Variations: unipolarity, higher voltages, greater speed <i>MOSFET transistor choices</i>	375	9x.9 Power Factor Correction (PFC)	418
		9x.10 High-Side High-Voltage Switching	421
		9x.11 High-Side Current Sensing	423

9x.11.1 Pulse generator overcurrent limit	423	9x.25.3 TVS devices <i>Gas surge arrestors; Metal oxide varistors; Zener TVSs</i>	475
9x.11.2 Current monitor for high-voltage amplifier	424	9x.25.4 MOV versus zener TVS	477
<i>Current monitor for HV bipolarity amplifier</i>		9x.25.5 “Series-mode” transient protection	478
9x.12 High-Voltage Discharge Circuit	427	9x.25.6 TVS circuit example <i>Fast-switching magnet</i>	479
9x.13 Beware Counterfeits (or, Don’t Bite into That Apple)	428	9x.25.7 Transient test circuit <i>Standard test pulses</i>	480
9x.14 Low-Noise Isolated Power	432	9x.25.8 Transient thermal response	482
9x.15 Low-Current Non-isolated DC Supplies	437	Parts Index	484
9x.15.1 Simplest circuit: reactance-limited zener bias	437	Subject Index	494
9x.15.2 Improved circuit: full-wave rectifier	437		
9x.15.3 Why hasn’t Silicon Valley responded?	438		
9x.15.4 Case study: ceiling fan	438		
9x.15.5 Inverse Marx generator	439		
9x.16 Bus Converter: the “DC Transformer”	442		
9x.16.1 Differences from classic switch-mode converter	442		
9x.16.2 Bus converter applications	442		
9x.16.3 Bus converter example	442		
9x.16.4 A few comments	443		
9x.17 Negative-Input Switching Converters	446		
9x.17.1 Negative buck from positive boost	446		
9x.17.2 Negative boost from positive buck	446		
9x.18 Precision Negative Bias Supply for Silicon Photomultipliers	448		
9x.19 High-Voltage Negative Regulator	450		
9x.20 The Capacitance Multiplier, Revisited	451		
9x.21 Precision Low-Noise Laboratory Power Supply	453		
9x.21.1 Overview	453		
9x.21.2 Circuit details	455		
9x.21.3 Performance	456		
9x.22 Lumens to Watts (Optical)	459		
9x.23 Sending Power on a Beam of Light	461		
9x.24 “It’s Too Hot” Redux	465		
9x.24.1 The finger test	465		
9x.24.2 Better thermometry	465		
9x.25 Transient Voltage Protection and Transient Thermal Response	474		
9x.25.1 The problem	474		
9x.25.2 The solution	474		